



BME

Budapest University of Technology and Economics



KJT

Faculty of Transportation Engineering and Vehicle Engineering

Department of Control for Transportation and Vehicle Systems

Electronics - electronic measuring systems

AC/DC circuits and circuit elements

Ernő Simonyi

simonyi.erno@sztaki.mta.hu

Previous Lesson


- Ohm's Law
 - $V = R * I$
- Kirchoff's Voltage Law
 - The algebraic sum of voltage around a closed loop is zero.
- Kirchoff's Current Law
 - The algebraic sum of all currents entering and leaving a node is zero.
- Voltage/current division

Sources (Generators)


Voltage and current sources

- Active circuit elements –they ‘create’ something
- Representation varies

Voltage sources

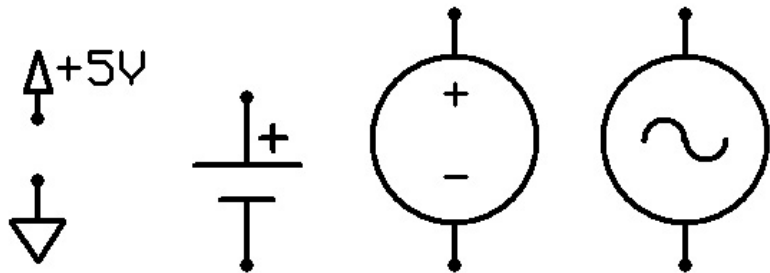

Current sources

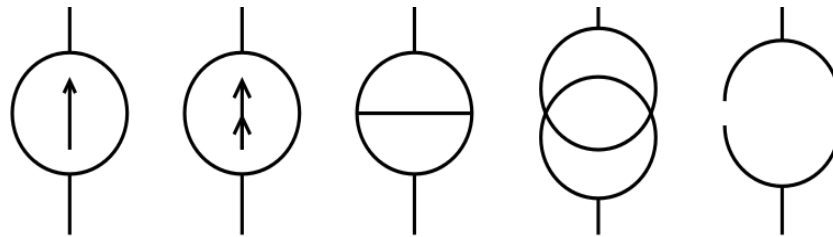


Sources (Generators)

How do you work with them

Superposition Theorem:

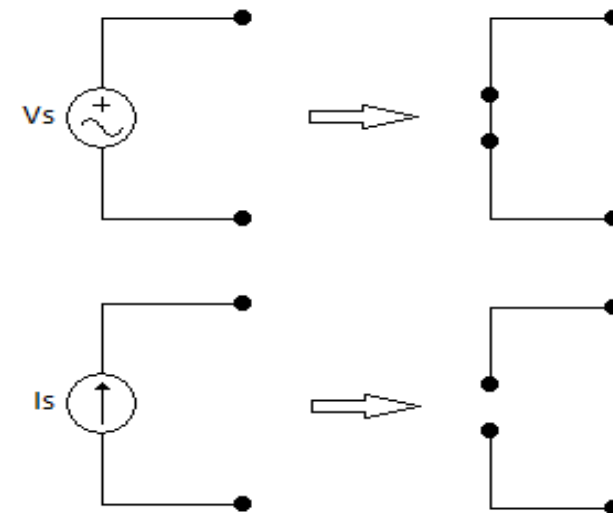- Total current through or voltage across a resistor or branch is the algebraic sum of the responses caused by each independent source acting alone.
- Keep one source
- Replace all other sources
- Resultant responses are added together



AC/DC

DC

- The electric charge (current) only flows in one direction.

AC

- Electronic charge changes direction **periodically** (in time).
- Voltage also reverses because of current changes direction.

AC/DC(2)

Generating AC

- Is produced using an alternator.
 - Special type of generator designed to produce AC
- A loop of wire is spun inside of a magnetic field,
- This induces a current along the wire.
- As the wire spins and enters a different magnetic polarity periodically, the voltage and current alternates on the wire.


Video link

AC/DC(3)

Budapest University of Technology and Economics




Faculty of Transportation Engineering and Vehicle Engineering

 Department of Control for Transportation and Vehicle Systems



AC/DC (4)

Waveforms

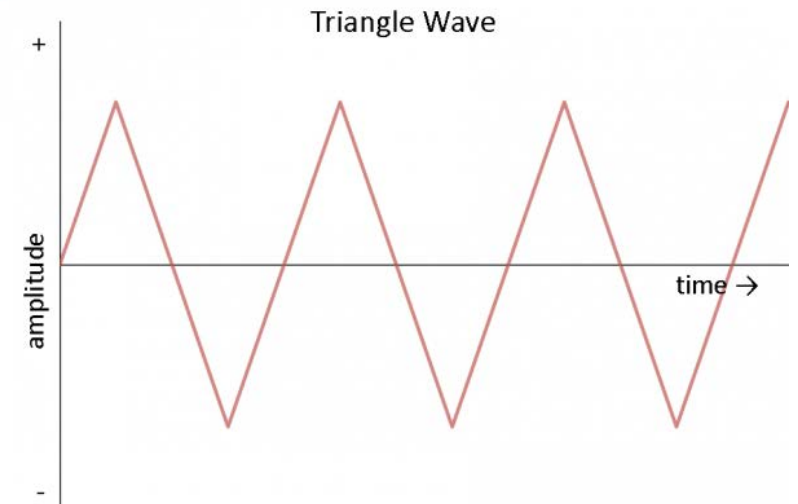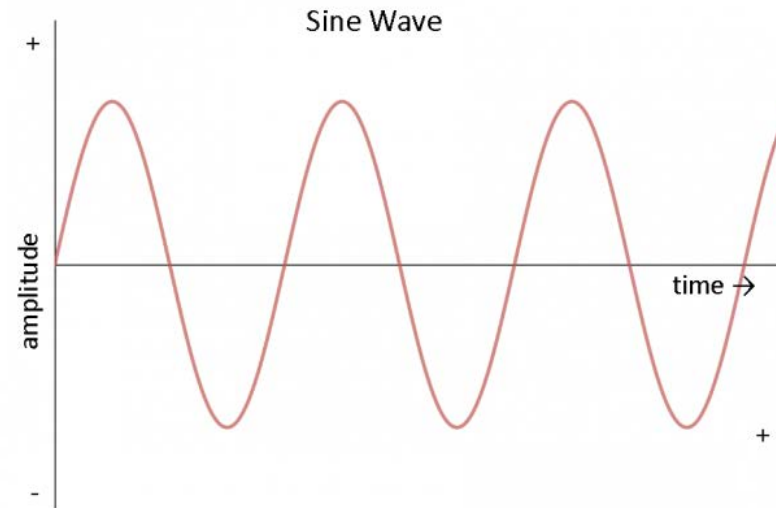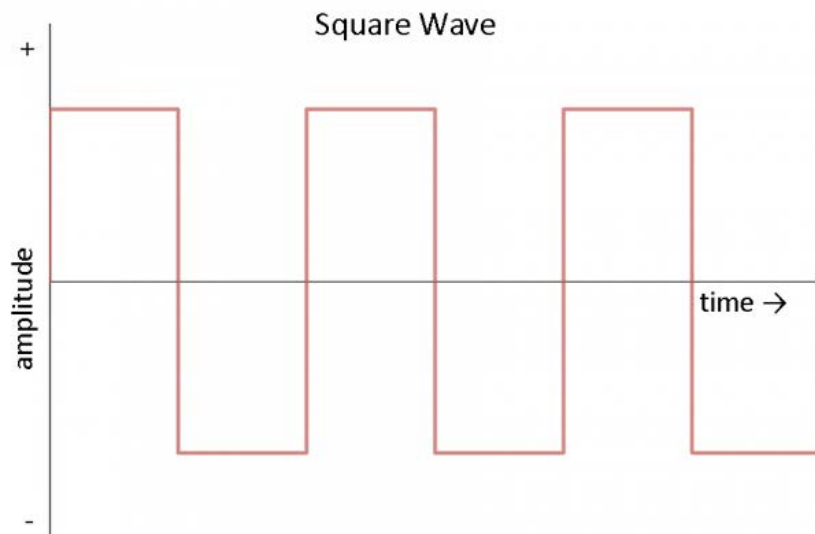

AC/DC (5)

How do we use AC circuit elements

- Ohm's and Kirchoff's laws still apply
- Vectorial representation on the complex plane
 - Rotating vector
 - Vector length (peak value)
 - Vector angle (phase)

Capacitors

- A capacitor is an energy storage element.
- It can store electrical pressure (voltage) for periods of time.
 - -When a capacitor has a difference in voltage (electrical pressure) across its plate, it is said to be charged.
 - -A capacitor is charged by having a one-way current flow through it for a period of time.
 - -It can be discharged by letting a current flow in the opposite direction out of the capacitor.

Capacitors(2)

On an ideal capacitor:

$$Q = C * V$$


C is the ability of a body to store an electric charge (unit: F - Farad)

The the V-I characteristic of a capacitor is:


$$I(t) = \frac{dQ}{dt} = C * \frac{dV}{dt}$$

Capacitors (3)


- A capacitor is constructed using a pair of parallel conducting plates separated by an insulating material (dielectric).
- When the two plates of a capacitor are connected to a voltage source as shown, charges are displaced from one side of the capacitor to the other side, thereby establishing an electric field.
- The charges continue to be displaced in this manner until the potential difference across the two plates is equal to the potential of voltage source.

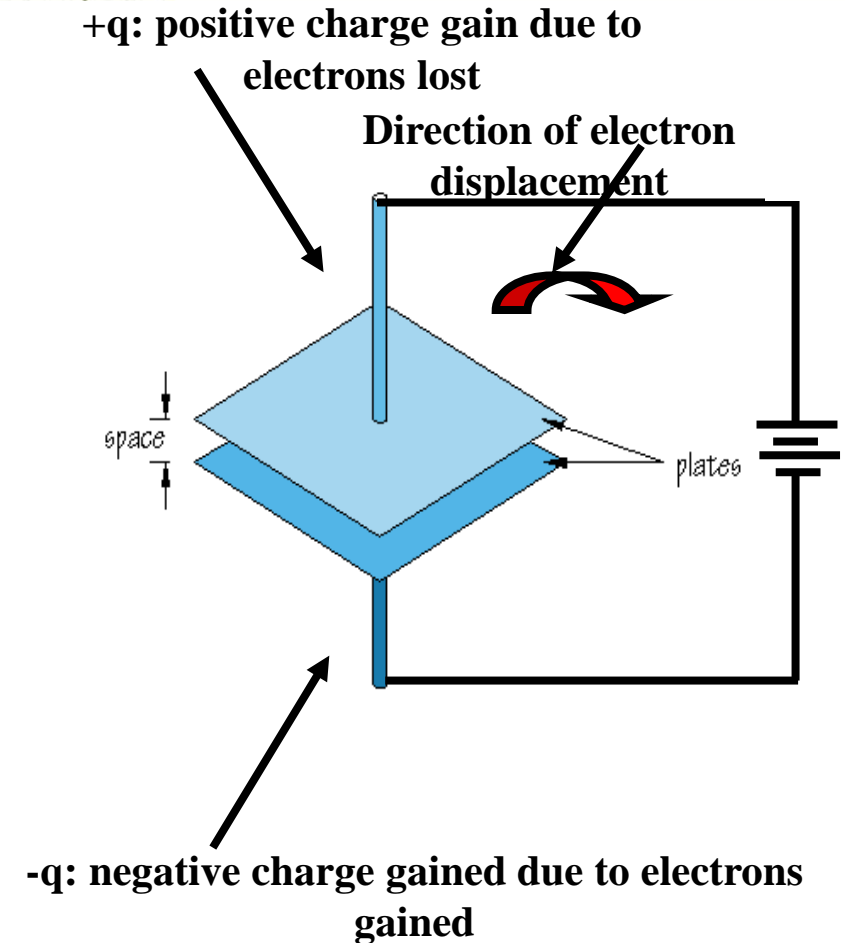


Capacitor symbols

 

**Fixed
capacitor**

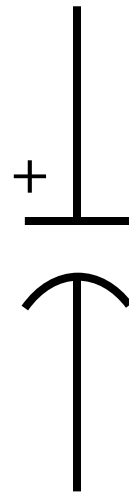


**Polarized
capacitor**

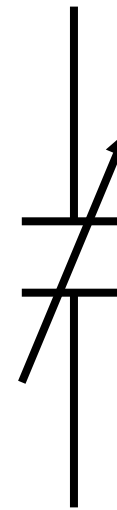

**Variable
capacitor**

Capacitor Reading Example

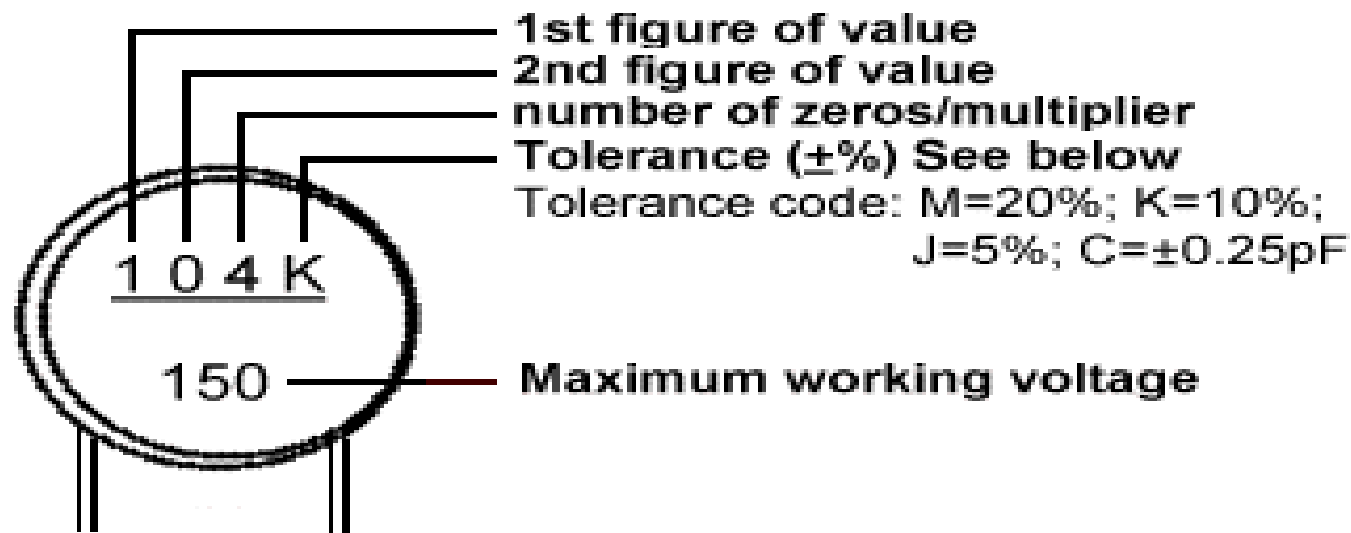

$$10 \times 10^4 \text{ pF} = 10^5 \times 10^{-12} \text{ F} = 10^{-7} \text{ F} = 0.1 \times 10^{-6} \text{ F} = 0.1 \mu\text{F}$$

• Thus, we have a $0.1 \mu\text{F}$ capacitor with $\pm 10\%$ tolerance.

Capacitor Variations



Inductors

- Inductor is a passive energy storage element that stores energy in the form of magnetic field.
- Inductor characteristic is governed by Faraday's law:

$$V(t) = \frac{d\lambda}{dt}$$

V = voltage induced across an inductor

λ = magnetic flux (unit: Webers, Wb) through the coil windings (a coil made using resistance-less wires) due to current flowing through inductor.

Inductors (2)

- For an ideal coil, magnetic flux is proportional to current, so

$$\lambda \sim I \text{ or } \lambda = LI$$

- L is constant of proportionality, called inductance (unit: Henry, Wb/Amp).
- So, now, the V-I characteristic of an inductor is:

$$V(t) = \frac{d}{dt}(\lambda) = \frac{d}{dt}(LI) = L \frac{dI}{dt}$$


$$I(t) = \frac{1}{L} \int_0^t V(\tau) d\tau$$

- The above V-I characteristics demonstrate that the current through an inductor can not be altered instantaneously.

Inductor symbols



Air core

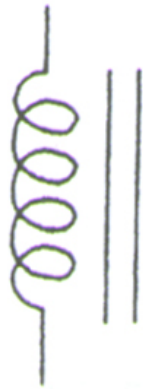

Iron core




Powered-iron
core




Variable
core

Inductor variations

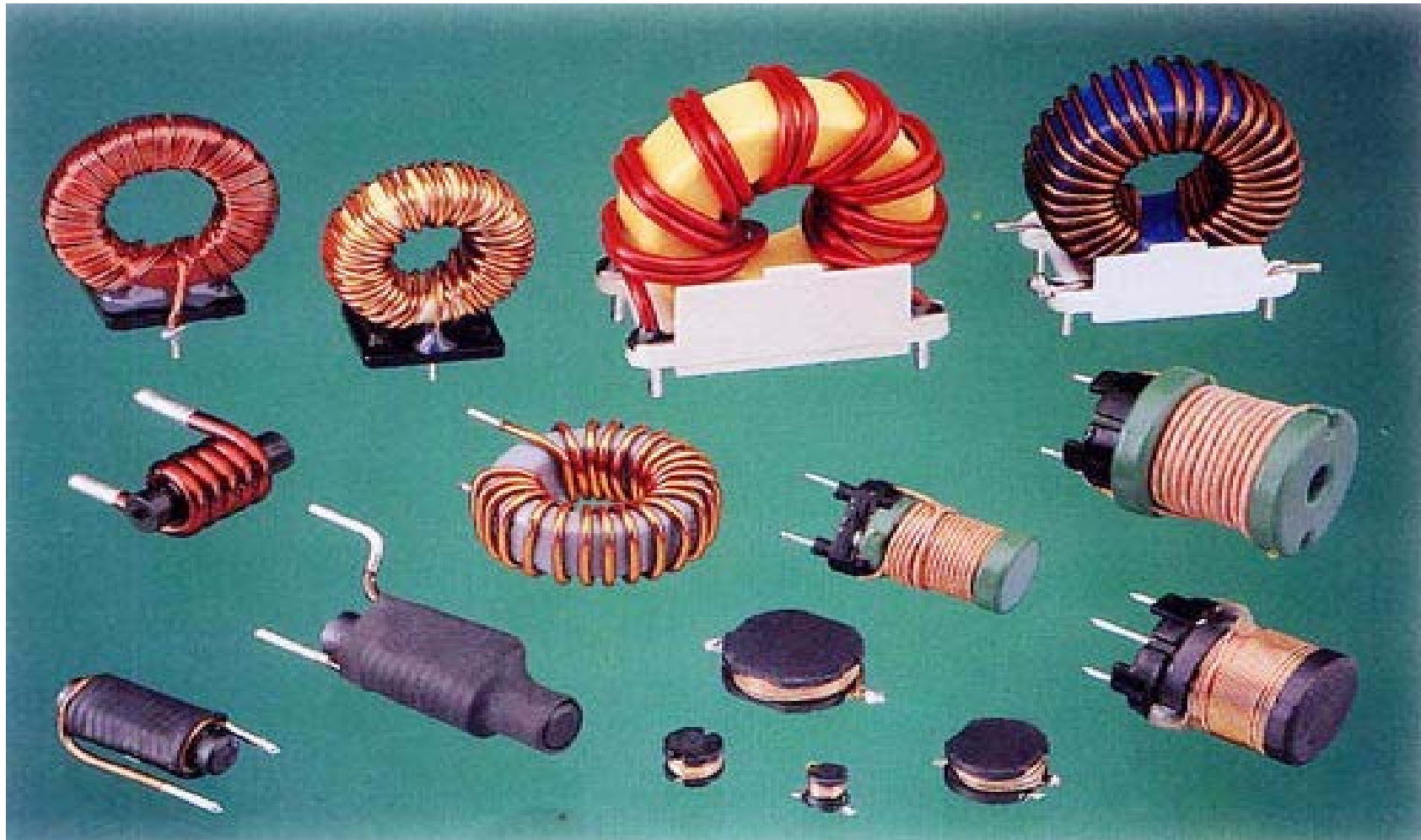

Measuring AC Voltage

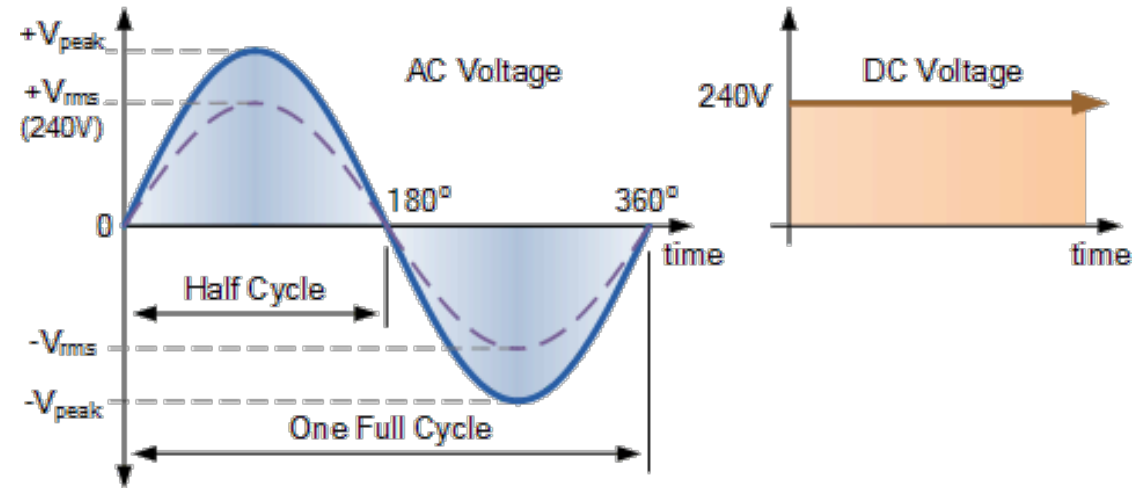- V_{peak} – peak to 0 voltage
- V_{pp} – peak to peak voltage
- V_{average}
- V_{RMS} – Root Mean Square voltage



- V_{RMS} - amount of AC power that produces the same heating effect as an equivalent DC power
- This is what gets measured on voltmeters (and ammeters)

Measuring AC Voltage(2)

- V_{RMS} calculation

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v(t)^2 dt}$$

- For sine waves only: $V_{rms} = V_{peak} * \frac{1}{\sqrt{2}} = V_{peak} * 0.7071$

Impedance

- Is defined as the frequency domain ratio of the voltage to the current.
 - In other words, it is the voltage–current ratio for a single complex exponential at a particular frequency ω .

- Polar form:

$$Z = |Z| e^{j \cdot \arg(Z)}$$


- the magnitude $|Z|$ represents the ratio of the voltage difference amplitude to the current amplitude
- the argument $\arg(Z)$ (commonly given the symbol theta) gives the phase difference between voltage and current.

Impedance(2)

- Cartesian form:

$$Z = R + jX$$

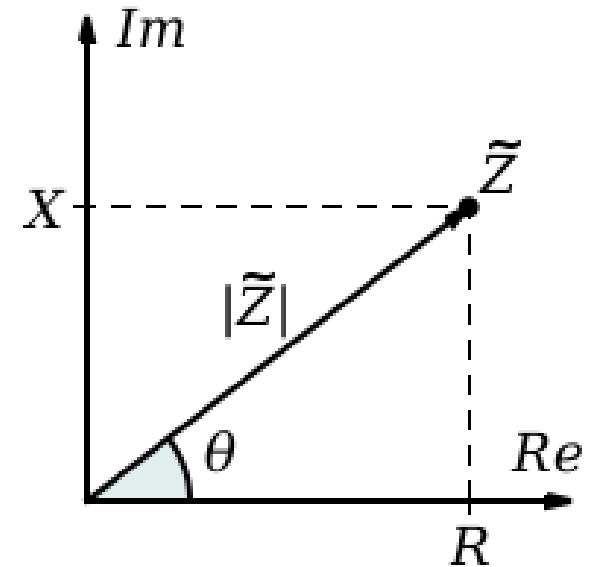- the real part of impedance is the resistance R
 - the imaginary part is the reactance X.
- Ohm' Law



$$V = I * Z = I * |Z|e^{j*arg(Z)}$$


Impedance and Phasors

Resistor

$$Z = R$$

Voltage – current are in phase

Pure resistive – no complex part

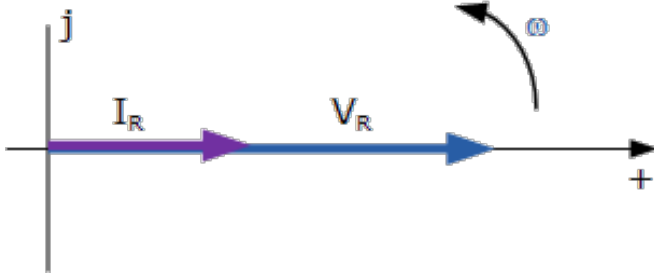

2018.10.29.


Capacitor

$$Z = \frac{1}{j\omega C}$$

Capacitive reactance

$$X_C = \frac{1}{\omega C}$$

Current leads voltage by 90°

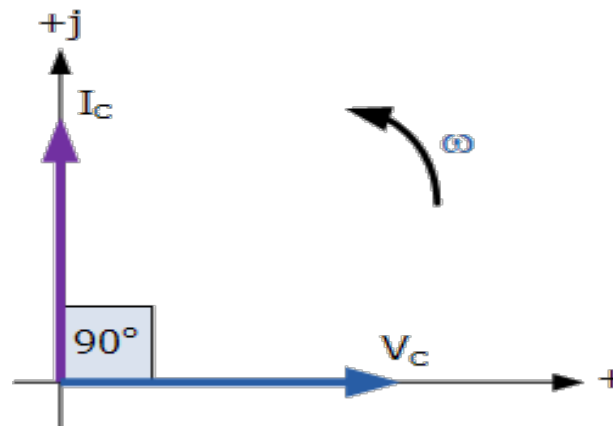

Inductance

$$Z = j\omega L$$

Inductive reactance

$$X_L = \omega L$$

Voltage leads current by 90°

