



**BME**

Budapest University of Technology and Economics



**KJIT**

Faculty of Transportation Engineering and Vehicle Engineering

Department of Control for Transportation and Vehicle Systems

# Electronics - electronic measuring systems

Transistor example, rectifiers, operational  
amplifiers


Ernő Simonyi

[simonyi.erno@sztaki.mta.hu](mailto:simonyi.erno@sztaki.mta.hu)
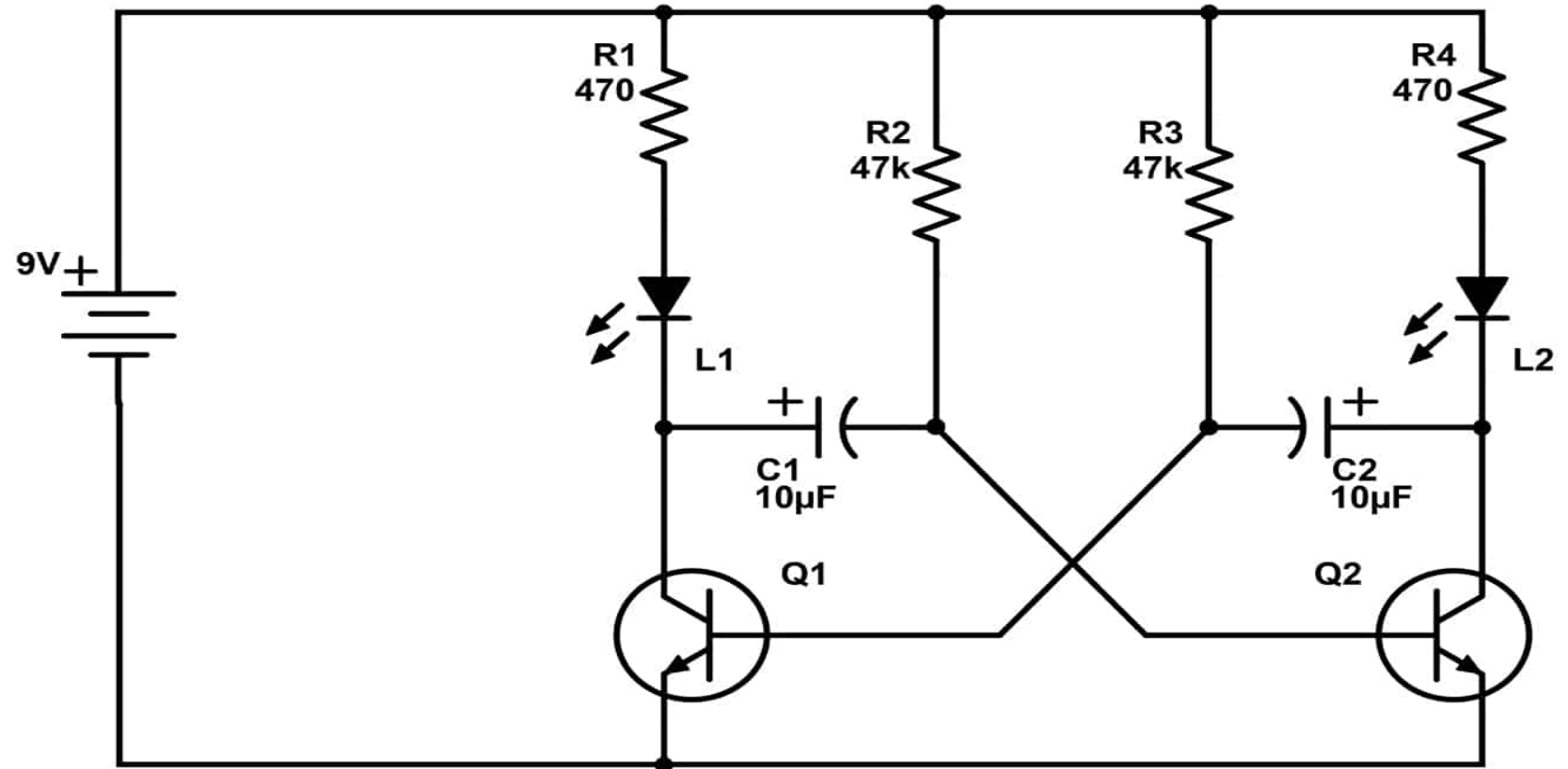
# Astable Multivibrator

The astable multivibrator circuit is a classic circuit for flashing two LEDs

- L1, L2 - LEDs
- R1,R4 - resistors to set LED current
- Q1, Q2 - transistors
- C1, C2 - capacitors
- R2, R3 - resistors



# Astable multivibrator (2)

- The Light-Emitting Diode (LED) on the left side is lit when the transistor on the left side (Q1) is ON.
- The LED on the right side is lit when the transistor on the right side (Q2) is ON.
- Both Q1, Q2 try to open at start, due to irregularities in the materials one will open faster.

# Astabil Multivibrator (3)

## Short explanation:

- The voltage on the left side of C2 controls transistor Q1.
- The voltage on the right side of C1 controls transistor Q2.
- When transistor Q1 turns ON, it changes the voltage of C1 so that Q2 turns off.
- After a short while, the voltage of C1 rises back up and turns on the transistor Q2.
- When transistor Q2 turns on, it changes the voltage of C2 so that Q1 turns off.
- This keeps repeating.

# Rectifiers




- Electrical device that converts alternating current (AC) to direct current (DC).
- Semiconductor diodes of various types (junction diodes, Schottky diodes, etc.).
- High-power rectifiers employ silicon semiconductor devices of various types (thyristors for example).
- Rectifiers may be single-phase or multi-phase.

# Rectifiers (2)

## Single-phase half-wave rectifier

- single-phase supply, either the positive or negative half of the AC wave is passed, while the other half is blocked
- one phase with a diode
- one half of the input waveform reaches the output

# Rectifiers (3)

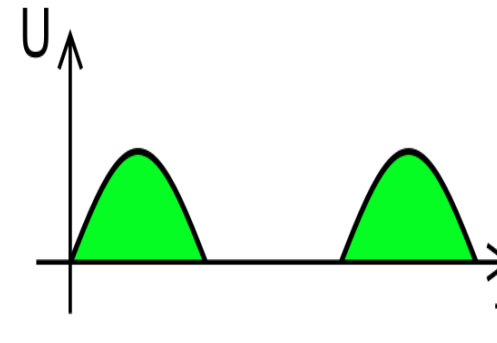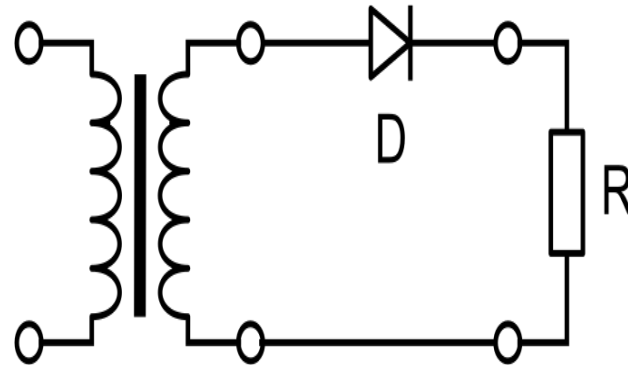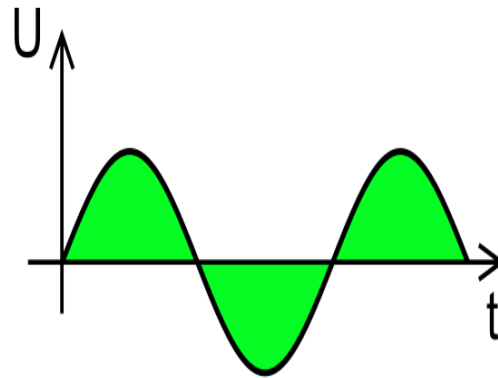

$$V_{dc} = \frac{V_{peak}}{\pi}$$

# Rectifiers (4)


## Single-phase full-wave rectifier

- whole of the input waveform to one of constant polarity (positive or negative) at its output
- two diodes and a center tapped transformer, or four diodes in a bridge configuration and any AC source
- Converts both polarities of the input waveform to pulsating DC








# Rectifiers (5)

- Graetz-bridge

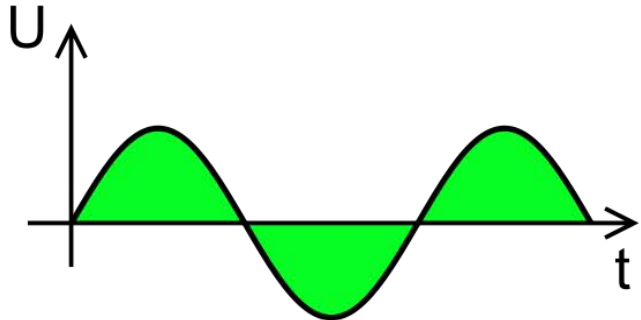


$$V_{dc} = \frac{2 * V_{peak}}{\pi}$$

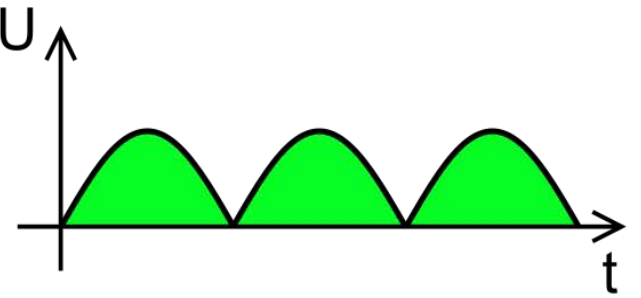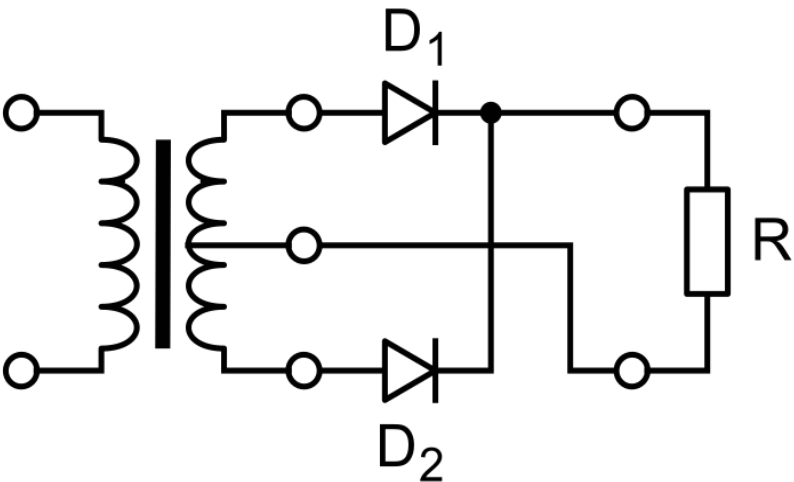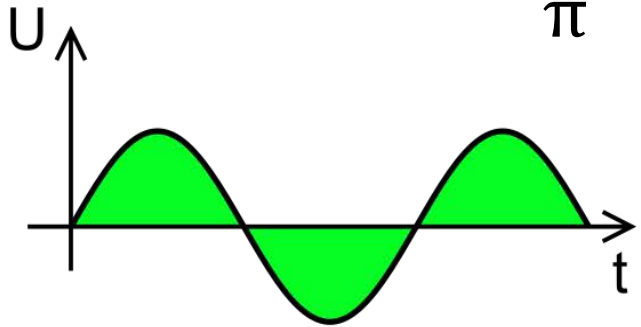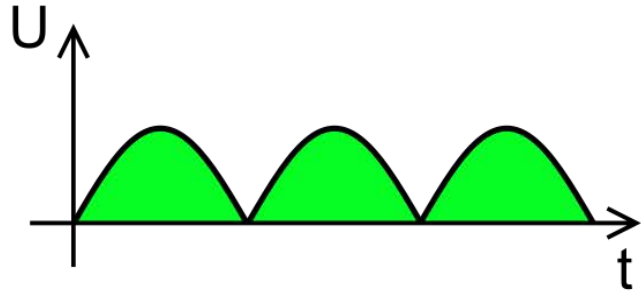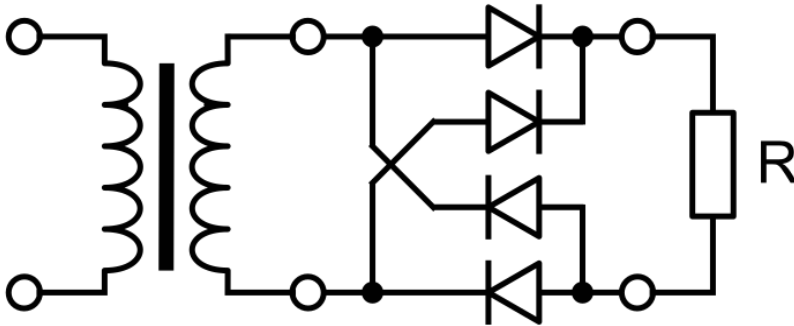

# Amplifiers


## Amplify input voltage or current

Operational  
amplifier

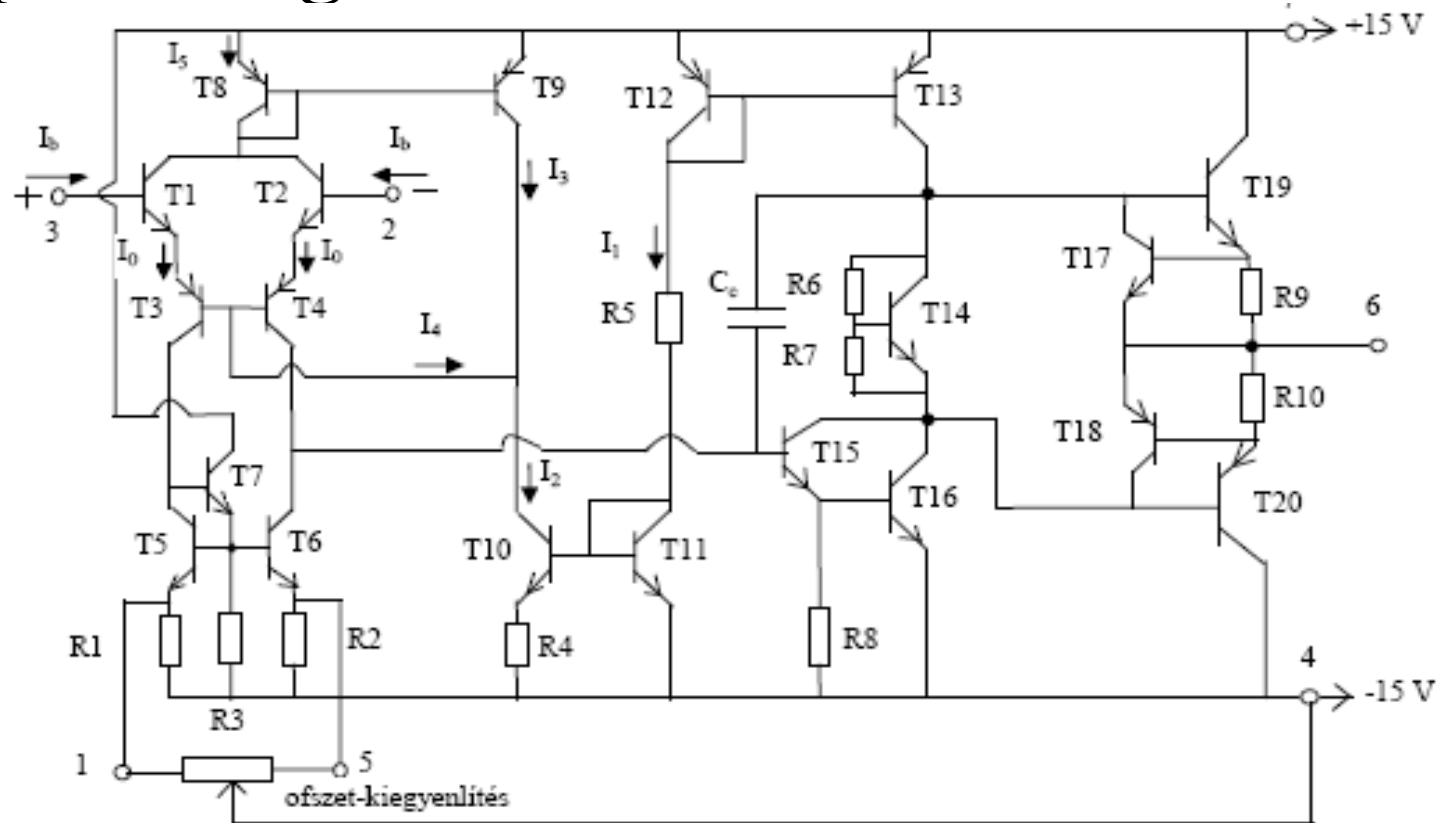

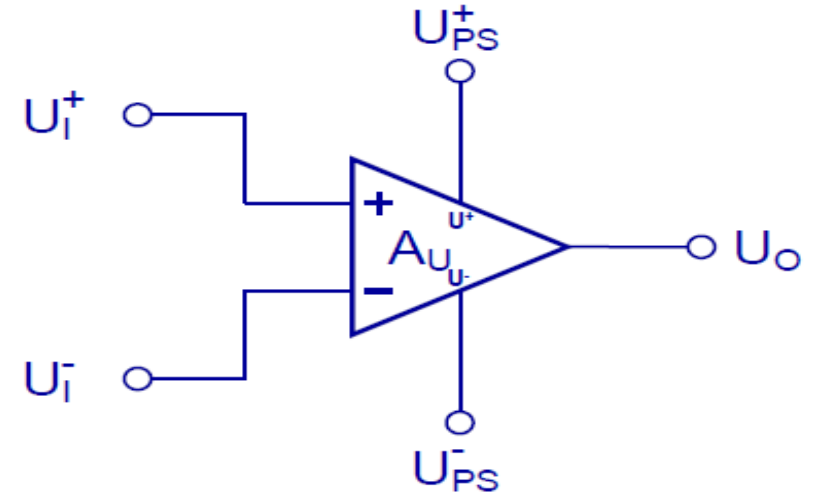
# Operational amplifiers

- Amplify small amplitude signals
- Signal manipulation
- Signal to noise (SNR) ration manipulation
- $U_o = A*(U_i^+ - U_i^-)$
- $A$  – voltage amplification (very large -  $10^4 - 10^8$ )
- No input current
- $R_b$  – input resistance (very large -  $10^4 - 10^8$ )




# Inverting amplifier

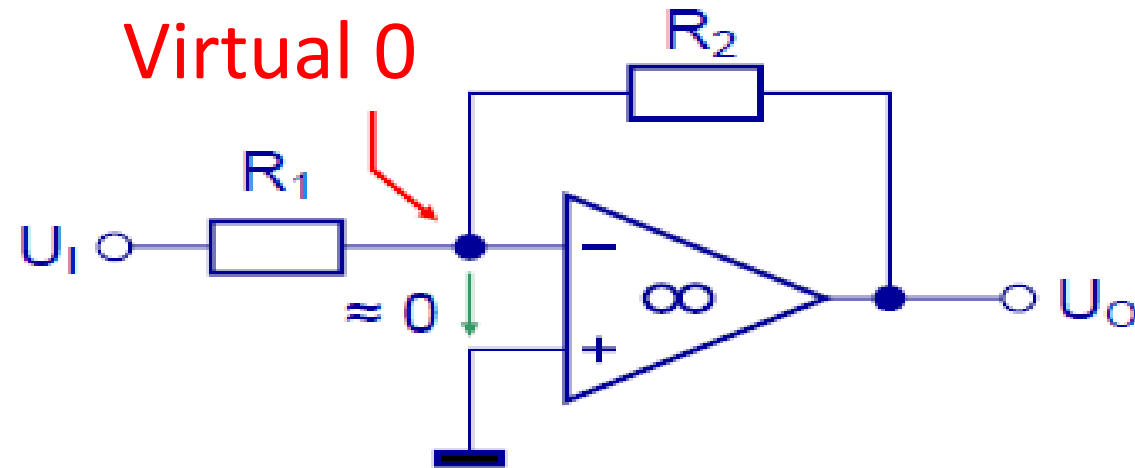


$$U_o = -\frac{R_2}{R_1} * U_i$$

# Non-inverting amplifier

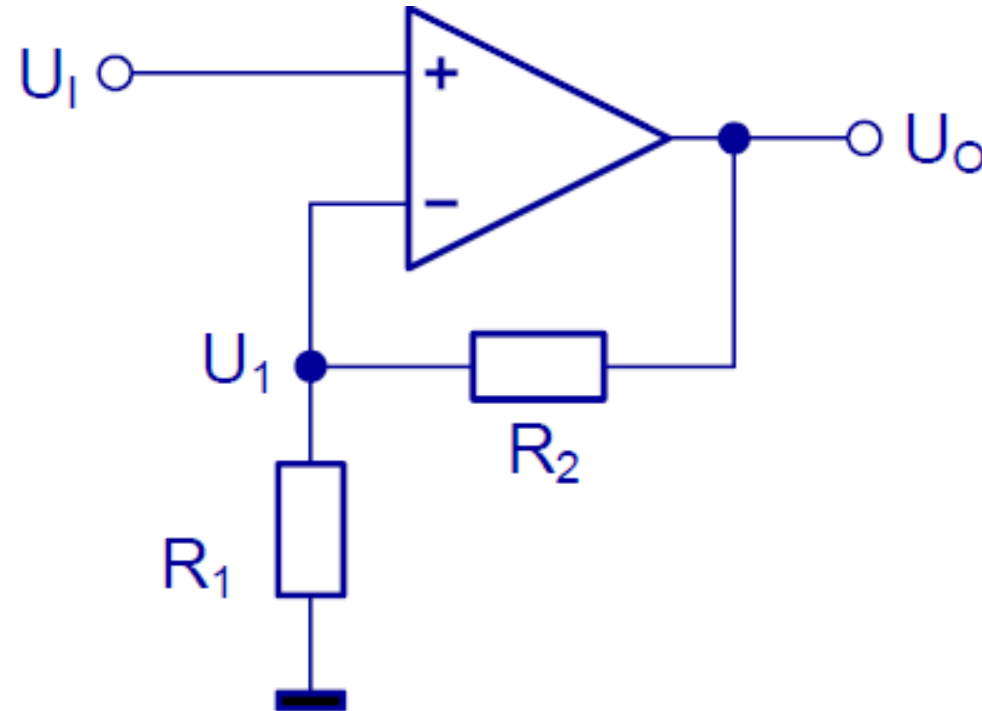

$$U_o = \left(1 + \frac{R_2}{R_1}\right) * U_i$$

# Integrator

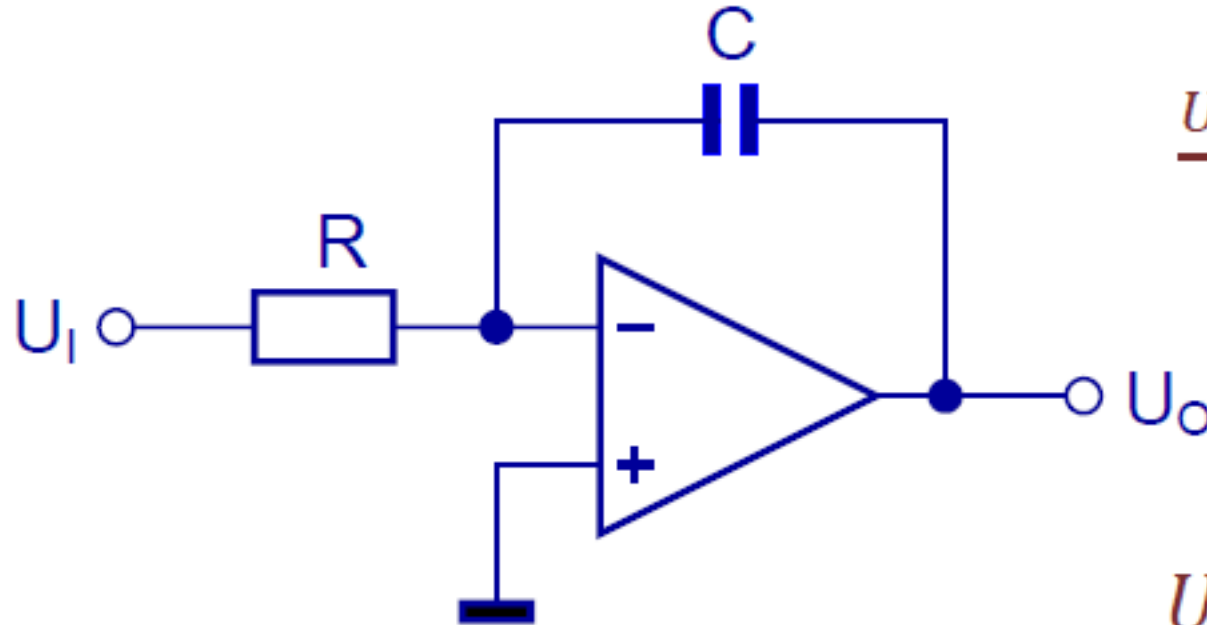

$$\frac{U_I(s)}{R} + sCU_O(s) = 0$$



$$U_O(s) = -\frac{1}{sRC} U_I(s)$$

$$U_O(t) = -\frac{1}{RC} \int_0^t U_I(\tau) d\tau$$